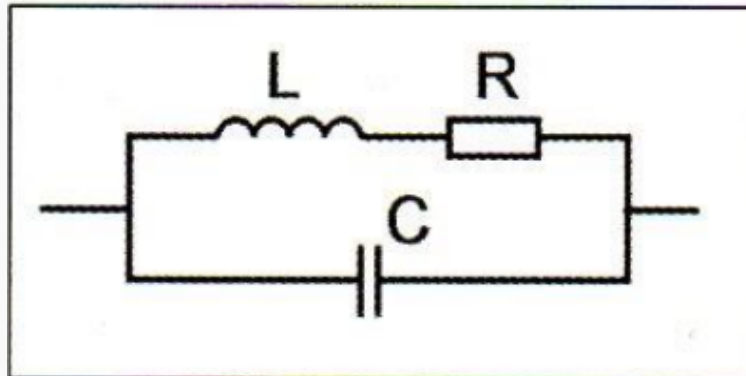


Understand the meaning of dynamic resistance, R_D ...



In this example, the inductor is $5\mu H$, the capacitor is $200pF$ and the resistor is 0.5Ω . Now calculate R_D , the dynamic resistance:

