3f.2 • Modulation modes and Linear Amplifiers • 000 • fea529e6

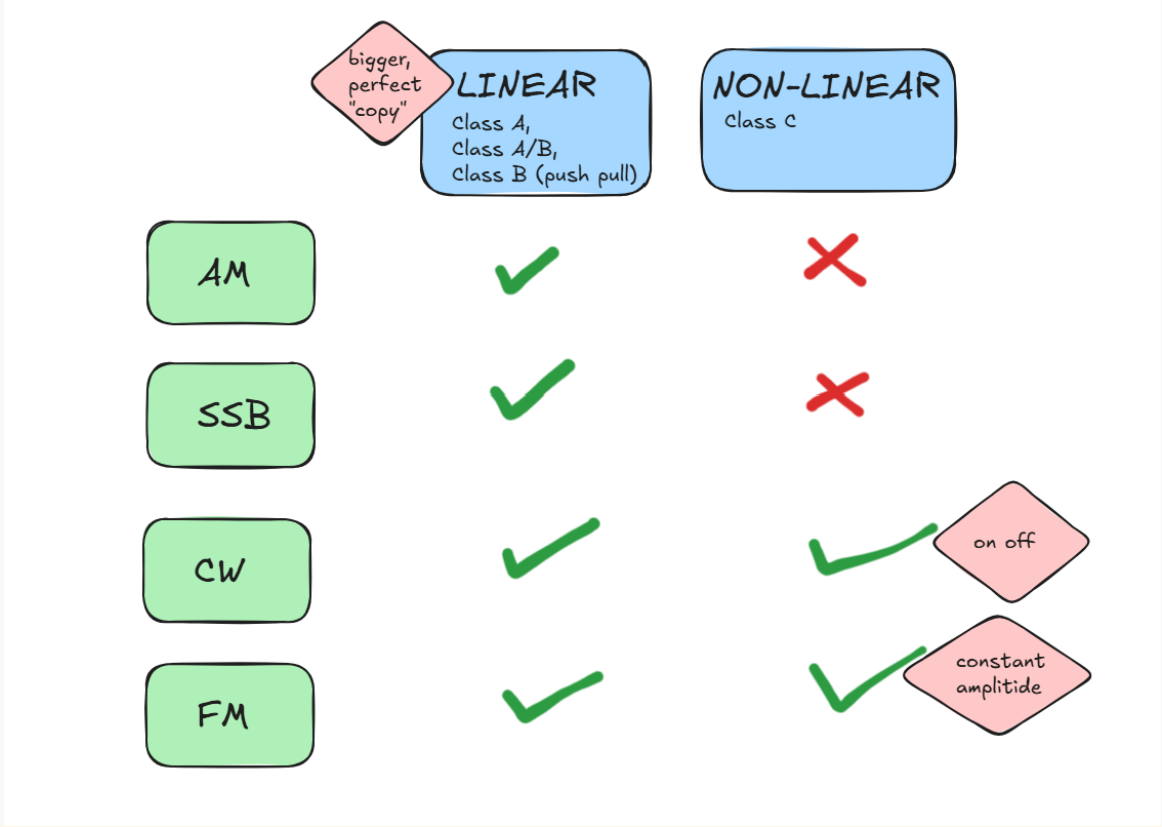

3f.2 • Modulation modes and Linear Amplifiers • 010 • 540229e6

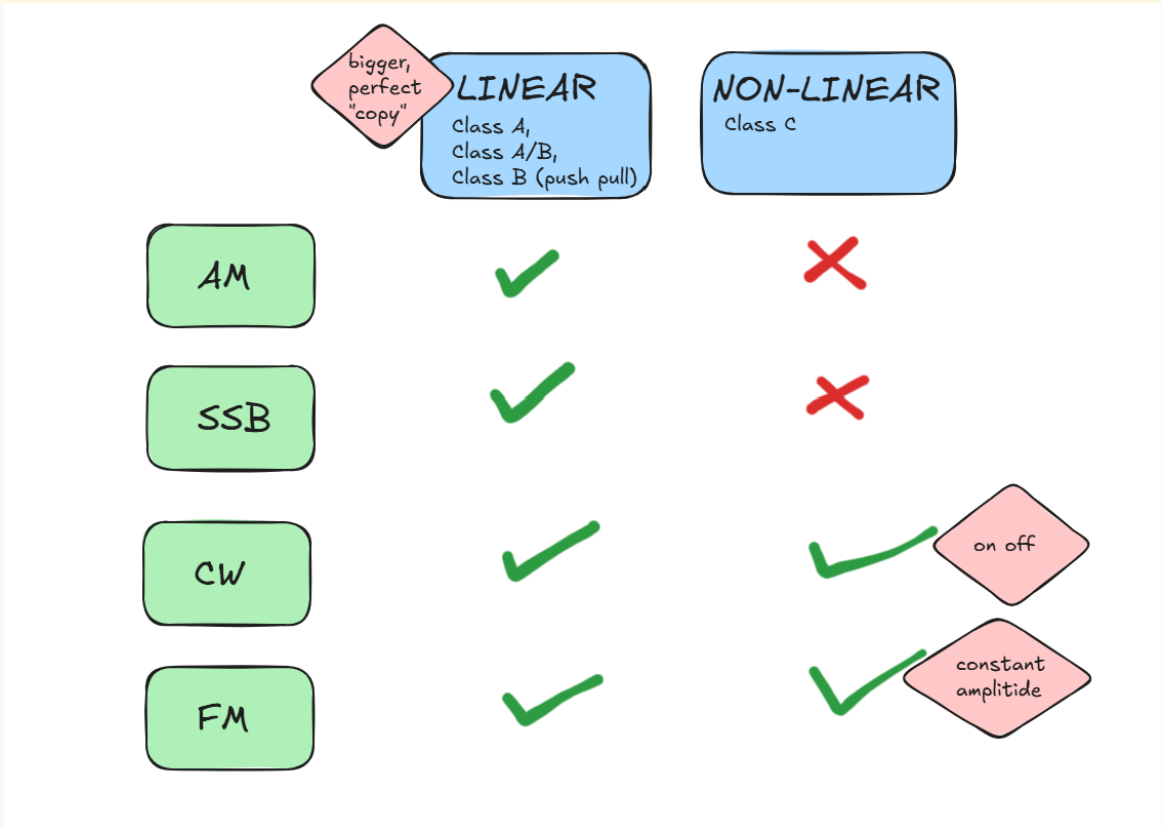

3f.2 • Linearity • 000 • 51bbdaaa

The output signal is a perfect copy of the input signal, with increased amplitude.

3f.2 • Calculating Mixer products • 000 • ac8dbbb7
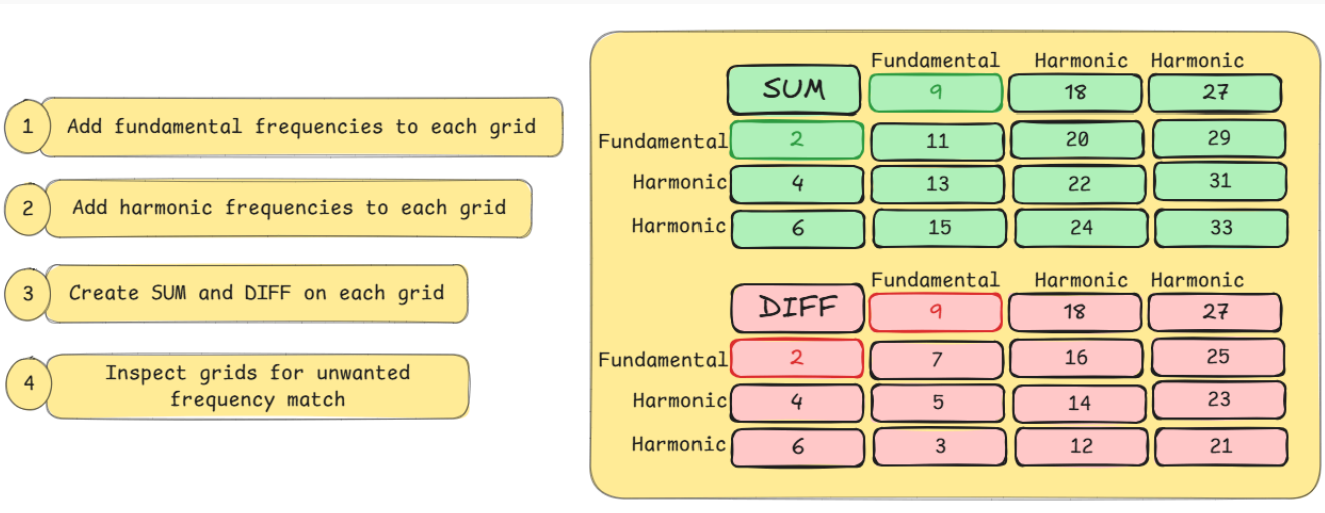
There is a 21MHz unwanted frequency on the DIFF worksheet.